More Circuit Identities

Solutions

Quick Exercises


1. Find different circuit that swaps qubits in the states $|+\rangle$ and $|-\rangle$, and show this is equivalent to the circuit shown above.

We have the single qubit gates at our disposal, and can only apply the two qubit gate CNOT.

We first prepare our states, gith q_0 in $|+\rangle$ state and q_1 in $|-\rangle$

Out[2]:

In [4]:

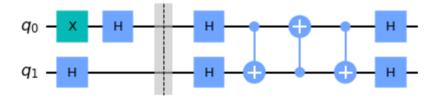

from qiskit textbook.tools import array to latex